

Exercise 4

Part 1 - Logic Functions

in0=switch1


in1=switch2

in2=switch3


out0=red

out1=yellow

out2=green

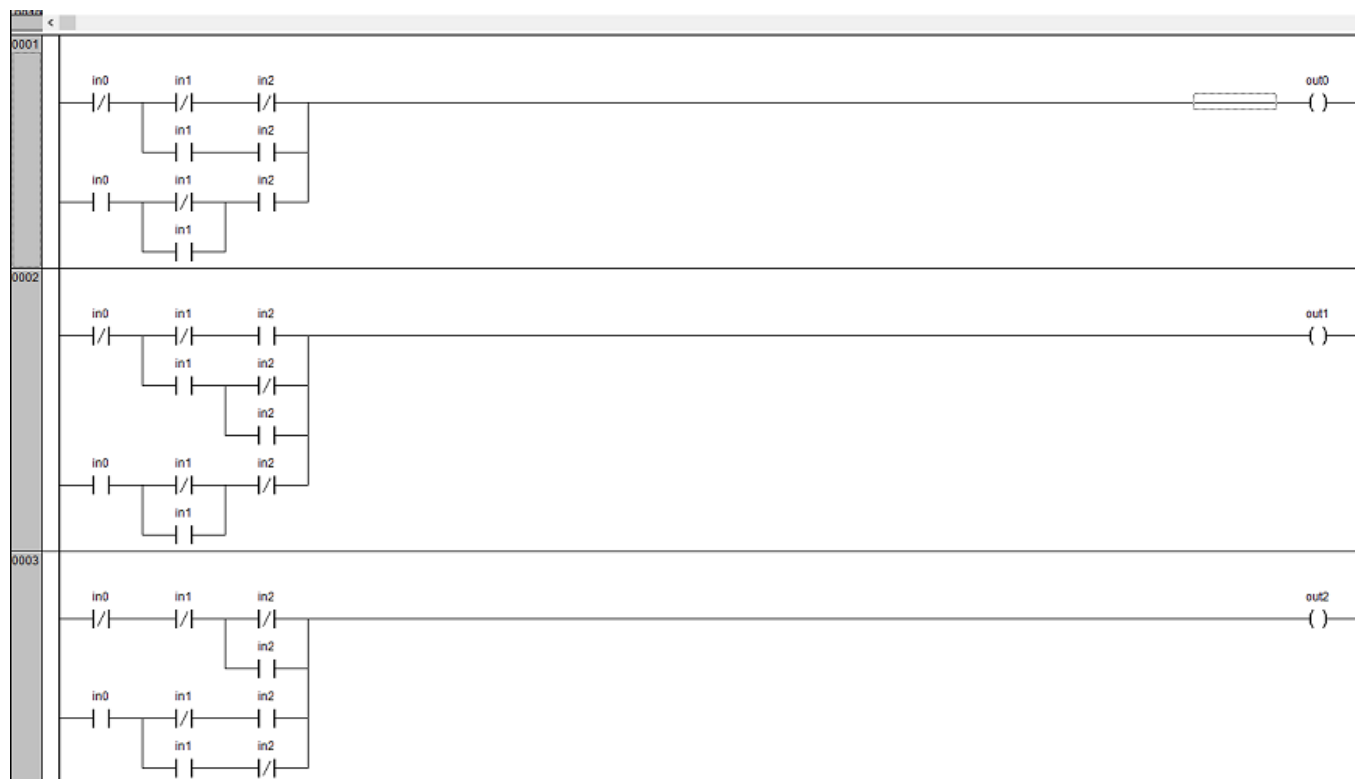

Conversion from ladder to FBD

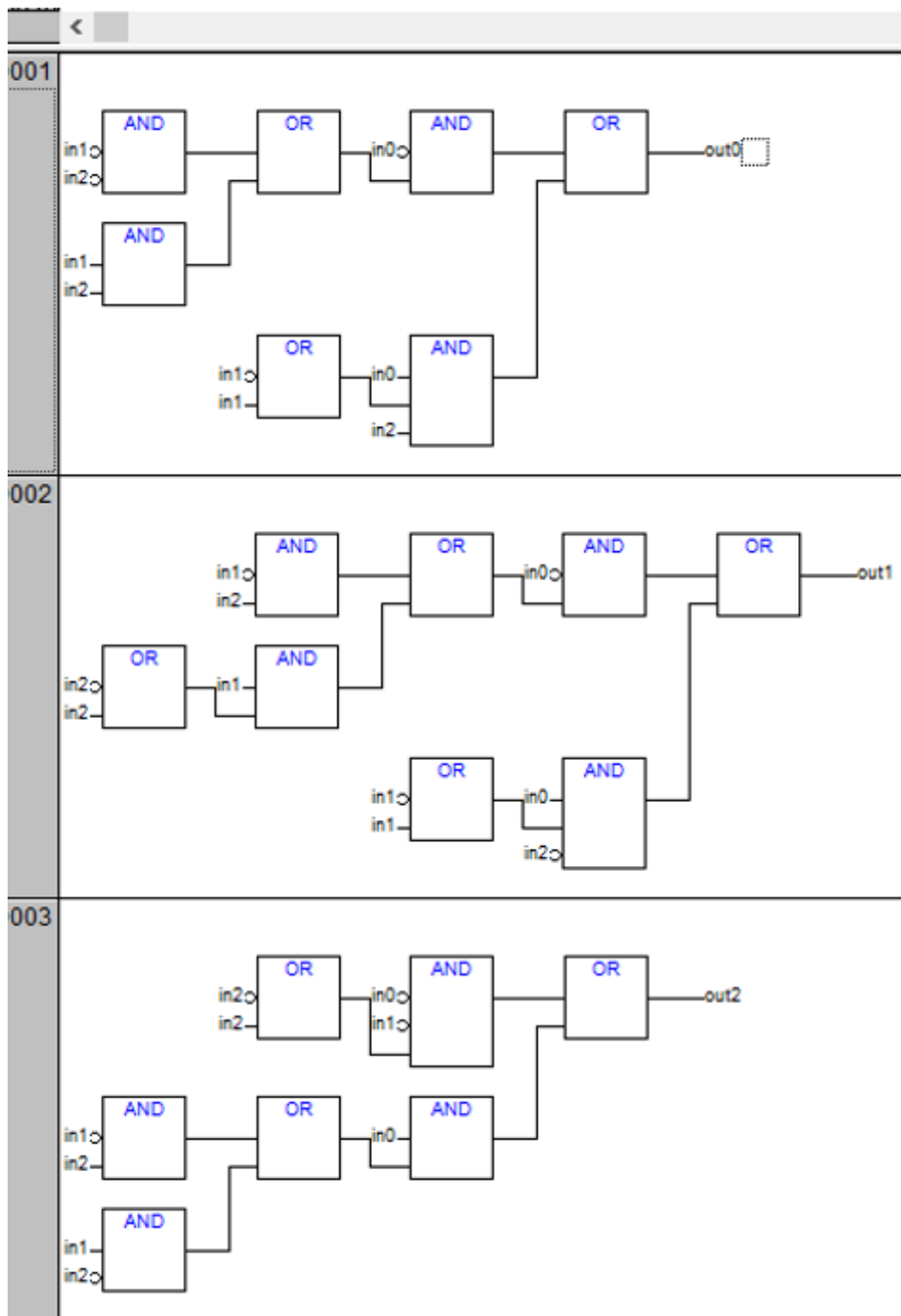


The FBD solution is correct.

Part 2 - Priority of Networks

The program given(below) does not work as intended because of the way the program reads the rungs. When **in0** is high, neither **out2** and **out0** is high, because they are also in rung2 and 3. When **in1** is high, **out2** is high and **out1** is low, because **out1** is in rung 3 which comes after rung 2. And when **in2** is high, **out1** and **out0** are high because there are no more rungs are rung 3 which contain these outputs.



One way to solve this problem is by setting up a truthtable of when the outputs are high and putting them in different rungs, like i have done below.

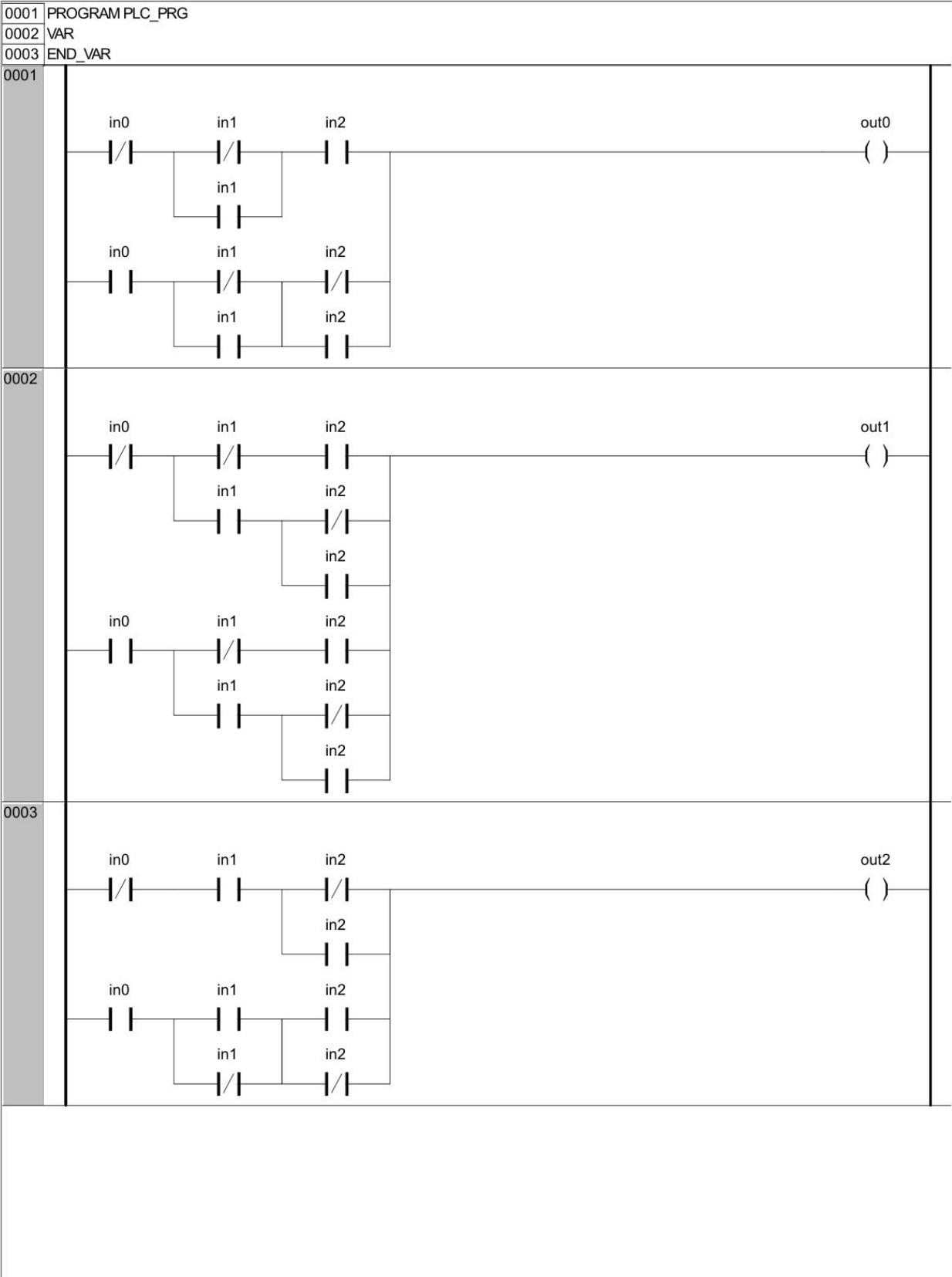

Part 3 - Retentive Coils

in0=switch1


in1=switch2

in2=switch3


out0=red

out2=green


Solution with normal coils.

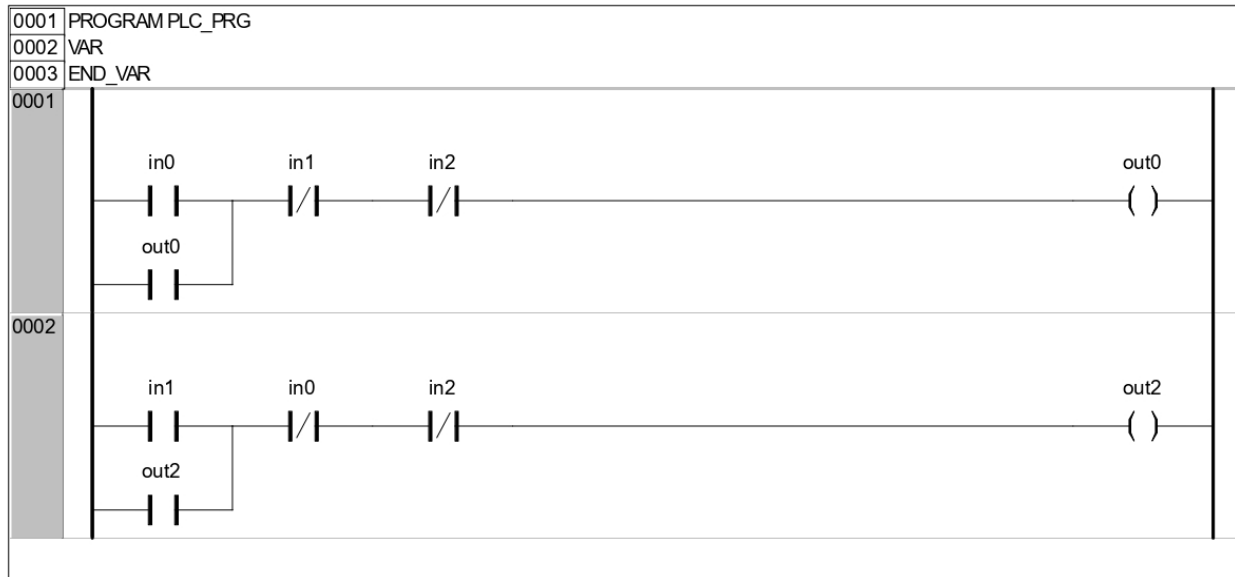


Solution with retentive coils.

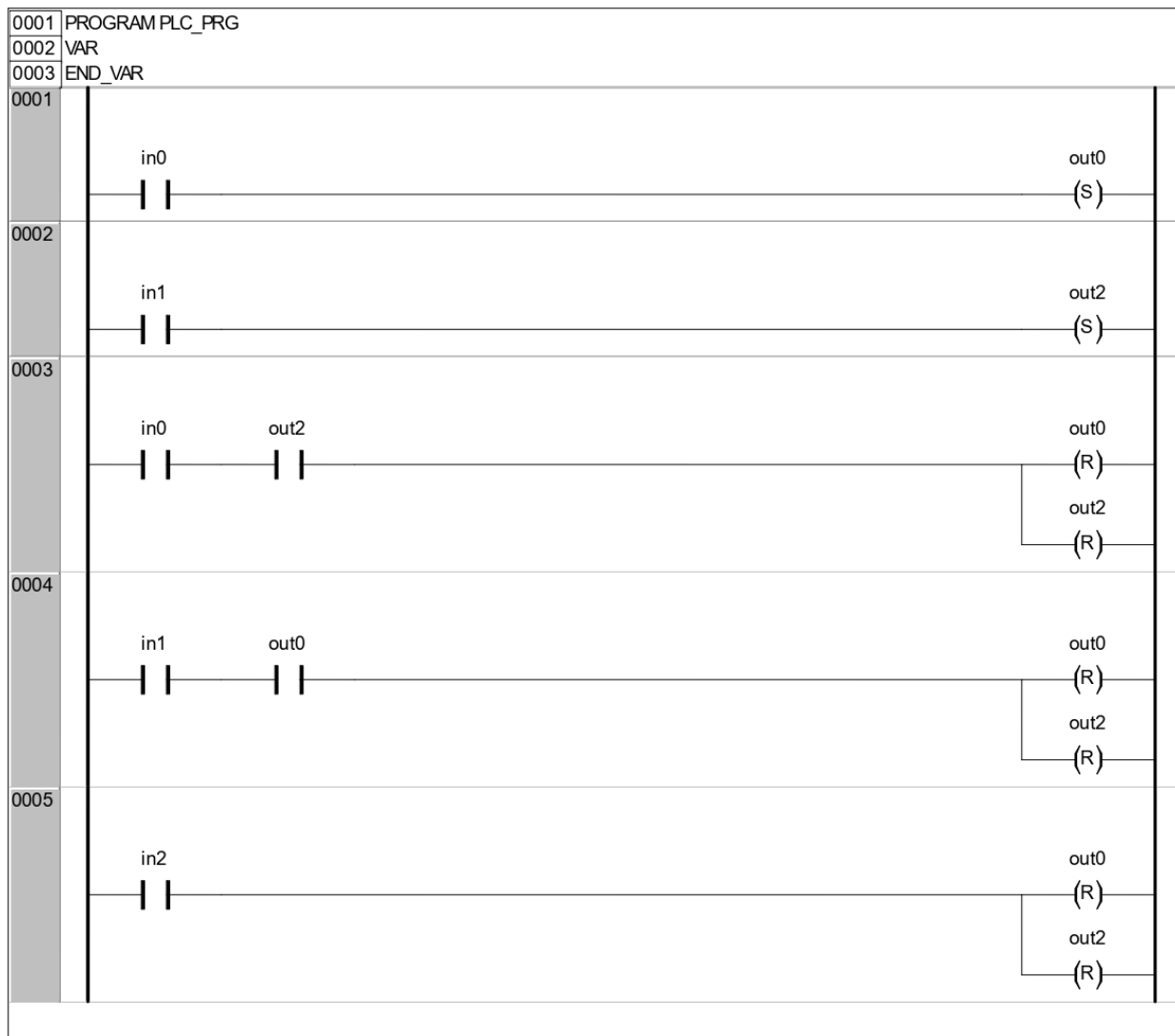

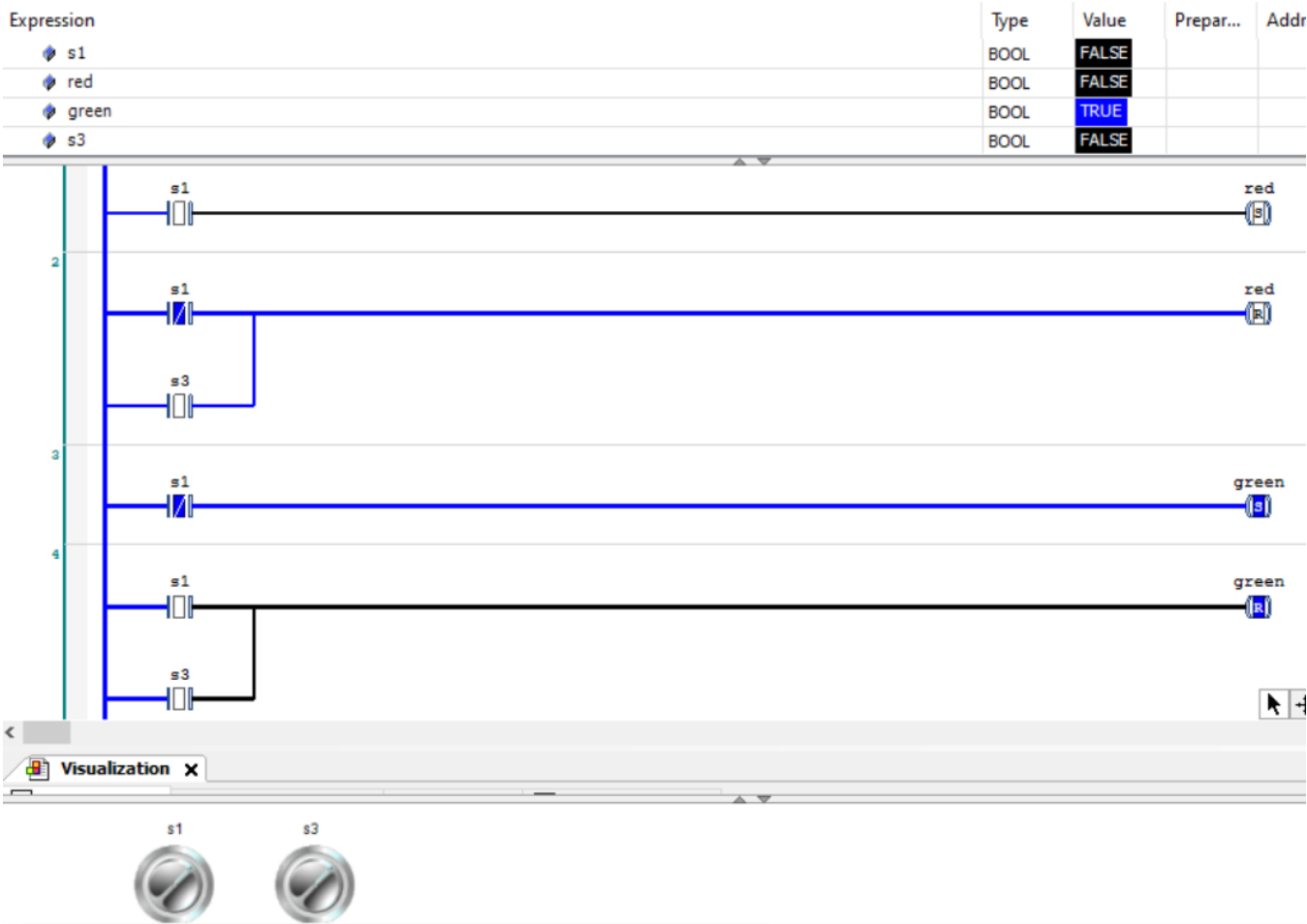The functionality can be achieved by only using one input switch. I have demonstrated this in a newer version of codesys on my computer using the simulation.




s1=low
s3=low

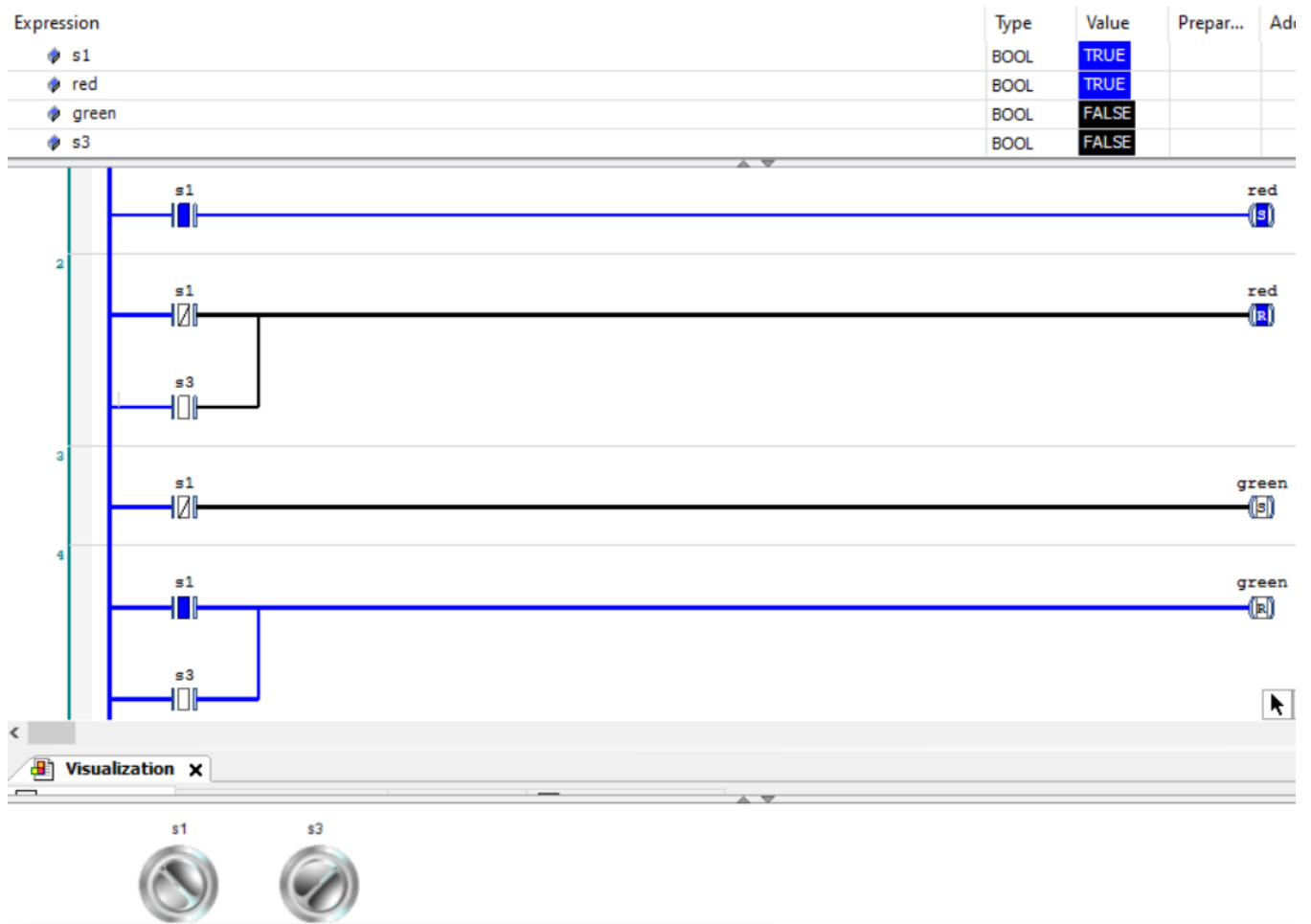


s1=high

s3=low

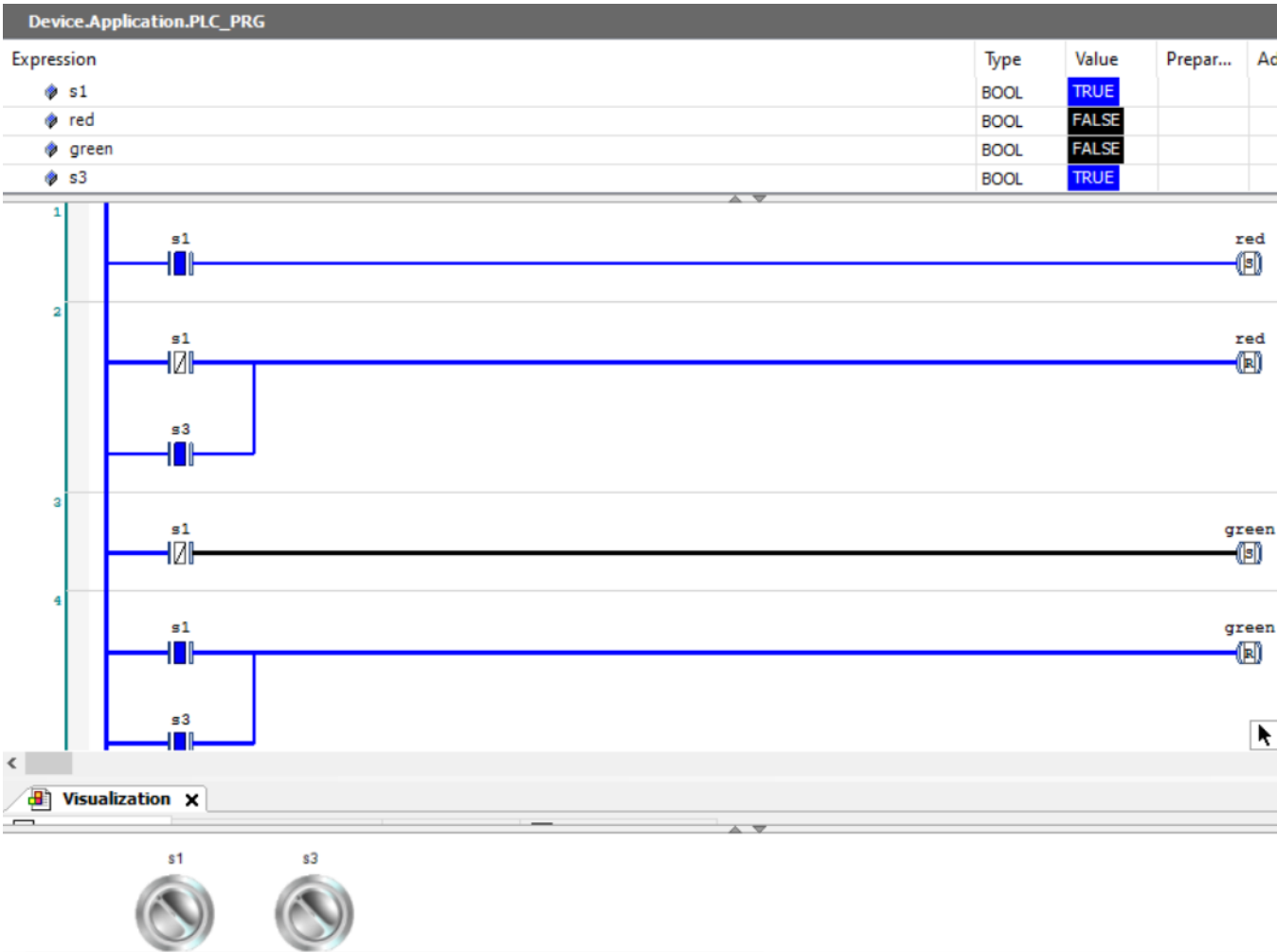

s1=high
s3=high

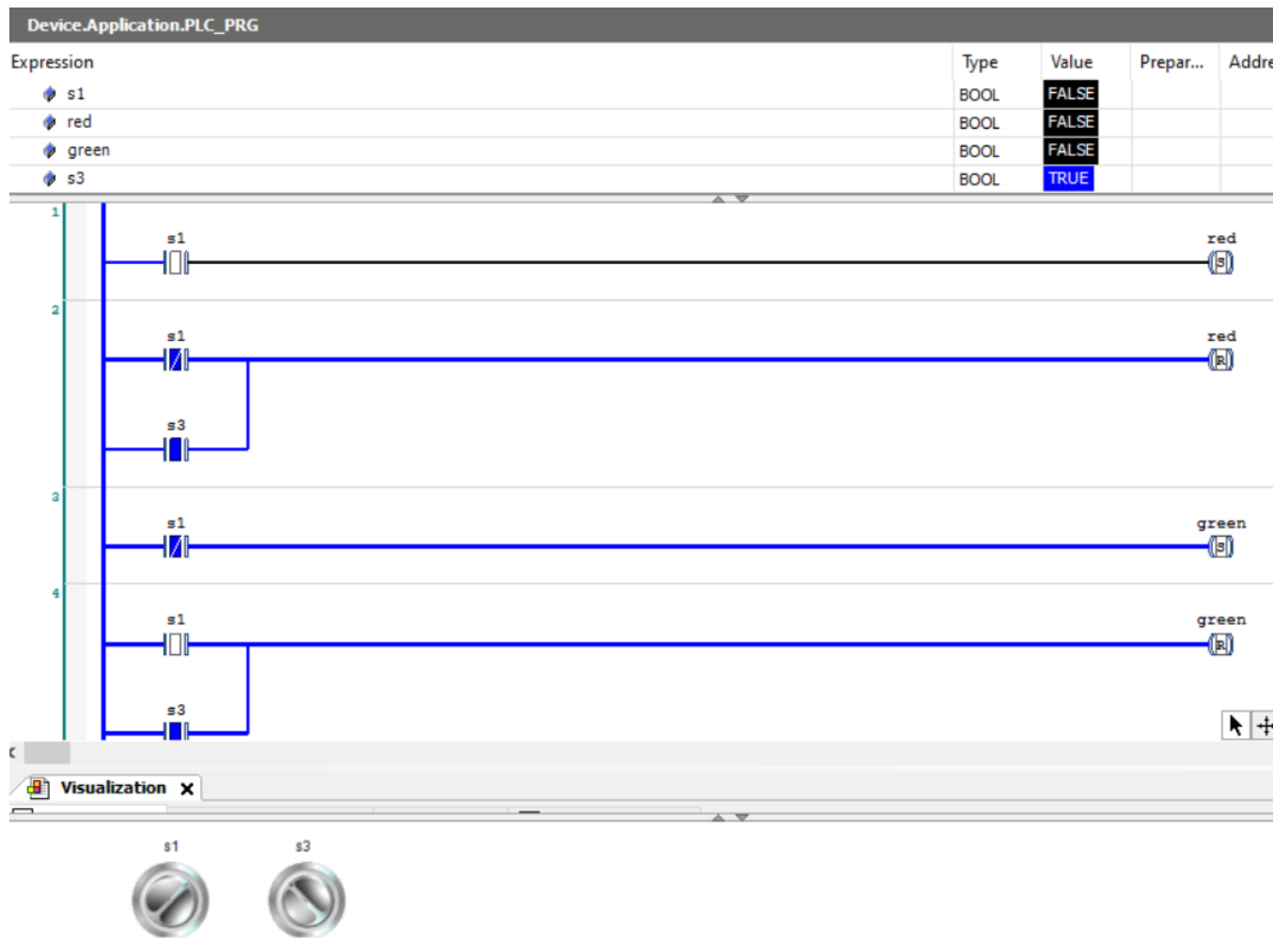

s1=low

s3=high

When s3 is high, both red and green are always low. If s1 is high and s3 low, output red is high and if s1 is low and s3 is low, out green is high.