
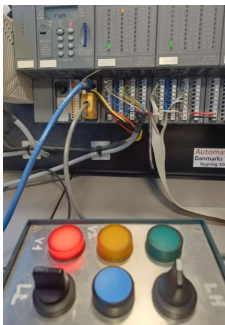



Basic Logic Functions

NAND

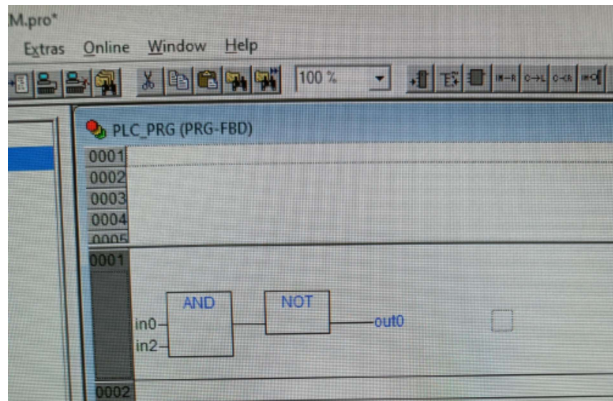
Jeg lavede den som en AND gate efter fulgt af en NOT gate. Men den kunne også laves som en ANDN, hvilket har samme funktion.




AND

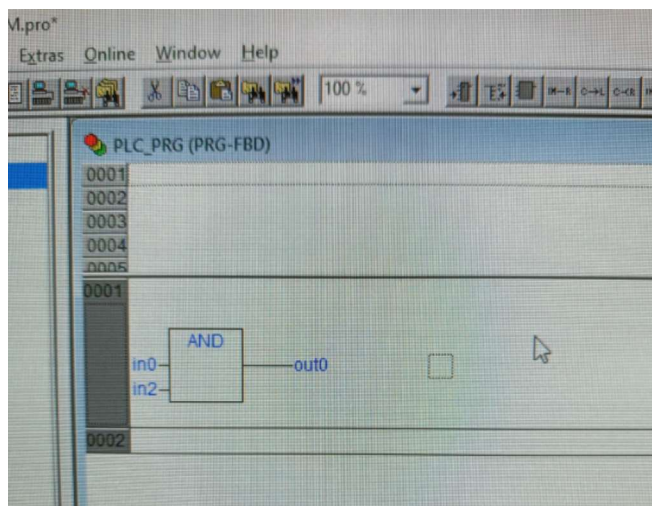

OR

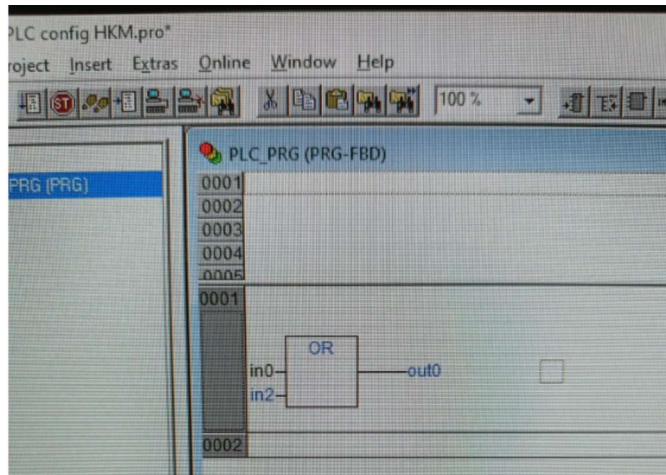


XOR

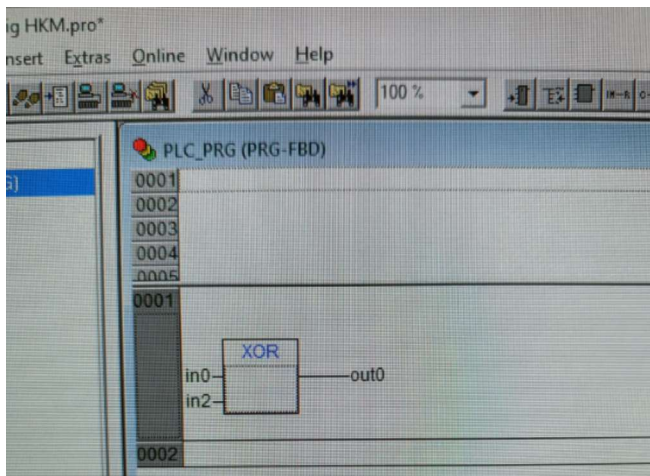

NOR

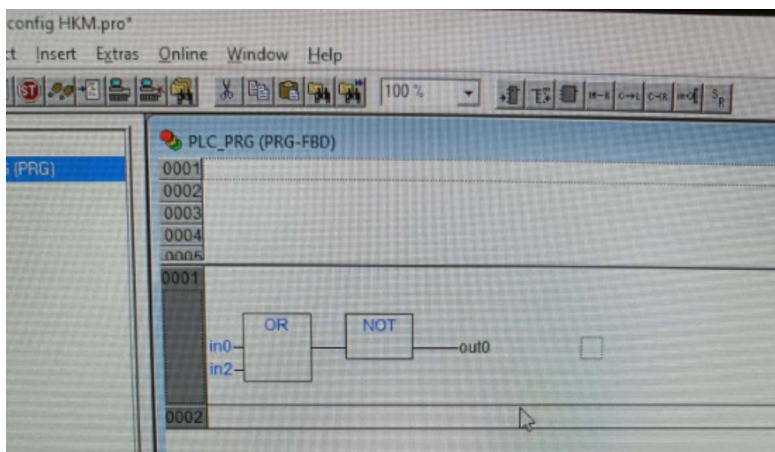Igen har jeg lavet den som en sammensætning af en OR gate og en NOT gate. Som ville være det samme som ORN.



Logic combination

		2	3		
Red					
1		00	01	11	10
	0	1	0	1	0
	1	0	0	1	0

$red = (\text{not } 1 \text{ and not } 2 \text{ and not } 3) \text{ or } (2 \text{ and } 3)$

with (Logic) :

simplify((not a and not b and not c) or (b and c))

$\text{not } (a \text{ or } b \text{ or } c) \text{ or } b \text{ and } c$

(2.1)

$red = \text{not}(1 \text{ or } 2 \text{ or } 3) \text{ or } (2 \text{ and } 3)$

		2	3		
yellow					
1		00	01	11	10
	0	0	1	1	1
	1	1	1	1	1

$yellow = 1 \text{ or } 2 \text{ or } 3$

		2	3		
green					
1		00	01	11	10
	0	0	1	0	1
	1	0	1	0	1


$green = (\text{not } 2 \text{ and } 3) \text{ or } (2 \text{ and not } 3)$

$green = 2 \text{ xor } 3$

out0 = red


out1 = yellow

out2 = green

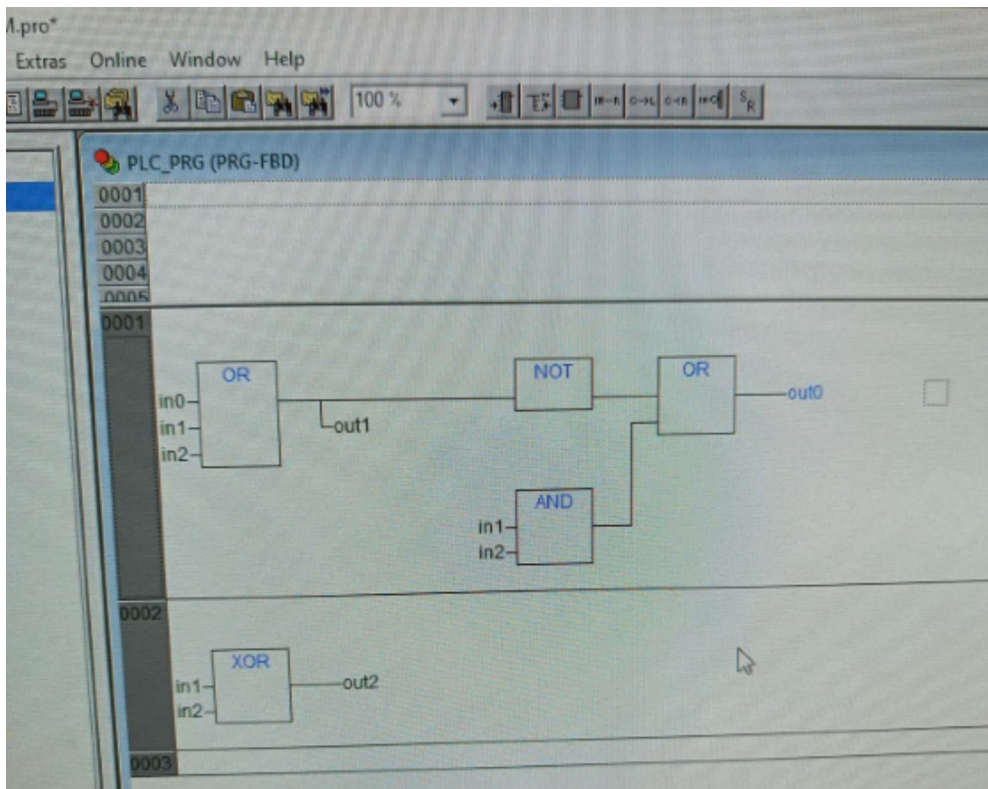

The number of logic gates necessary to implement this is 1xOR3, 1xNOT, 1xOR2, 1xAND, 1xXOR gate.

Latch

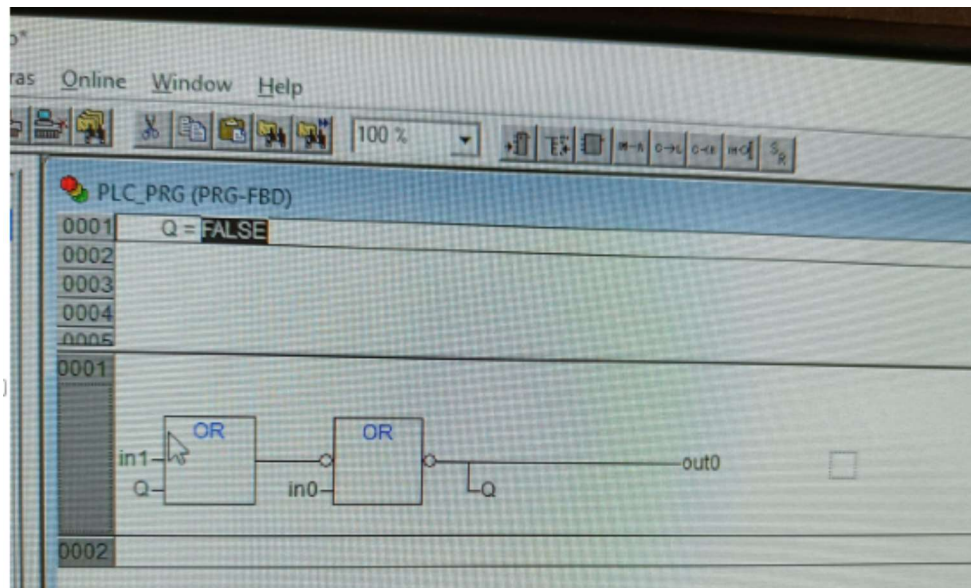

in1 is the middle push button.
 in0 is the first switch button.
 out0 = red LED

Timers

